

# Full bridge converter

## *Transformers and isolated converters*


Most DC power supplies have the following requirements:

1. Regulated output voltage  
Solved by a large capacitor at the output, and feedback control.
2. High power factor  
PFC - discussed previously.
3. Isolation
4. Multiple outputs

Isolated topologies include transformers, which easily solve the two latter requirements, as we will see.

### Transformers


A transformer consists of two or more coils that are magnetically coupled (a common magnetic flux flows through them). Usually, the coils are windings around a common magnetic core, as shown in Figure 1.

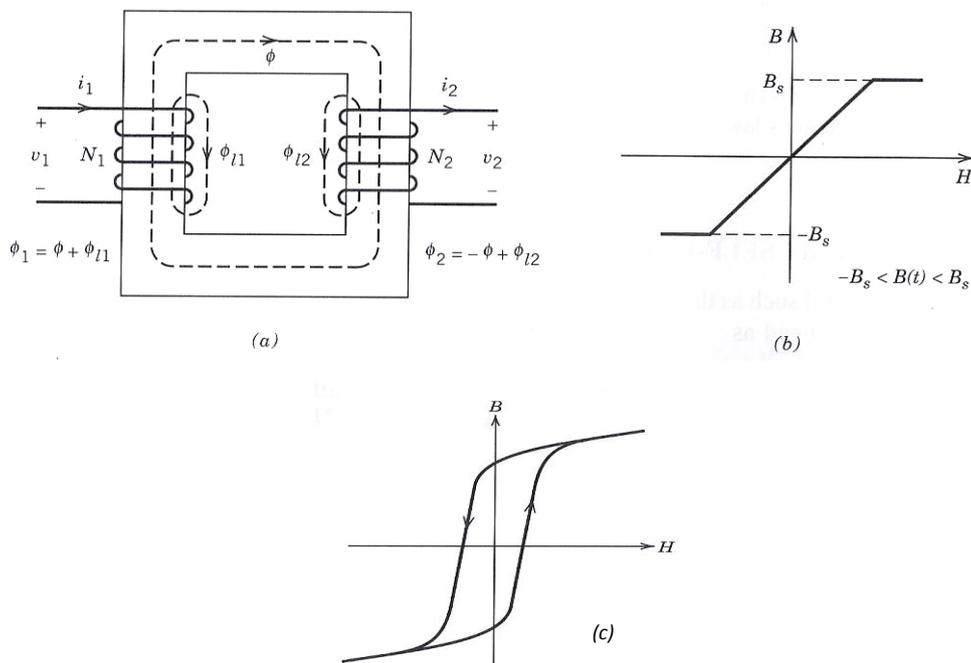

**Fig. 1: (a) cross section of a transformer. (b) Ideal  $B$ - $H$  characteristics of the core. (c)  $B$ - $H$  characteristics of the core with hysteresis.**

Figure 2 shows the equivalent circuit of a transformer. Ideal transformers (Figure 2(b)) have the following properties:

1. No conduction losses in the windings ( $R_1 = R_2 = 0$ ).
2. Infinite core permeability ( $L_m = \infty$ ).
3. No leakage fluxes ( $L_{l1} = L_{l2} = 0$ ).

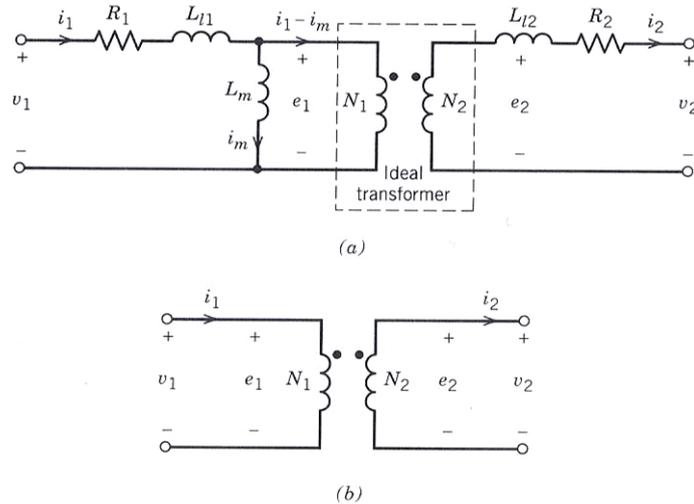


**Fig. 2: (a) Equivalent circuit for a non-ideal transformer with a lossless core and no hysteresis. (b) Equivalent circuit for an ideal transformer.**

In an ideal transformer, the current and voltage in both side are:

$$\frac{i_1}{i_2} = \frac{N_2}{N_1}, \quad \frac{v_1}{v_2} = \frac{N_1}{N_2}.$$

- Since there is no electrical connection between the two sides of the transformer (only magnetic one), it is *isolated*.
- Multiple outputs can be created by having multiple windings (in addition to the secondary winding), as shown in Figure 3.

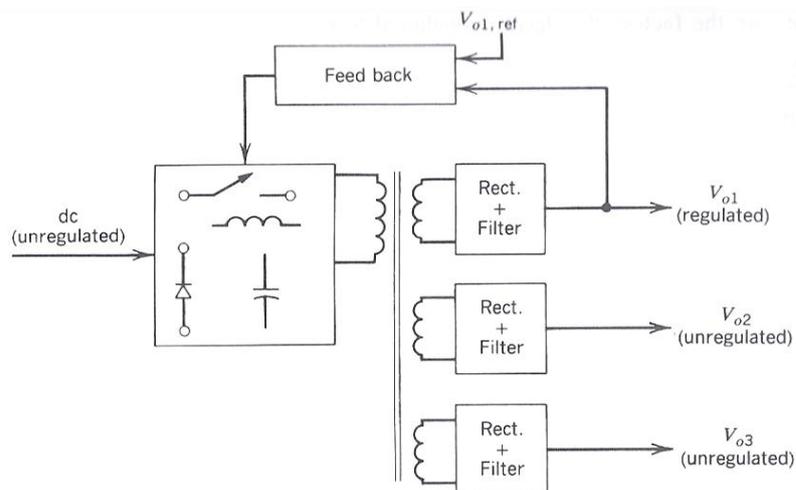


**Fig. 3: Multiple outputs**

There are two kinds of isolated converter topologies:

1. Unidirectional core excitation – only the positive part of the  $B-H$  curve is used.  
Include: Flyback converter (shown in the lecture by Prof. Weiss), forward converter.
2. Bidirectional core excitation – both positive and negative parts of the  $B-H$  curve are used. Include: push-pull, half-bridge, full-bridge (explained below).

### An example - full-bridge converter

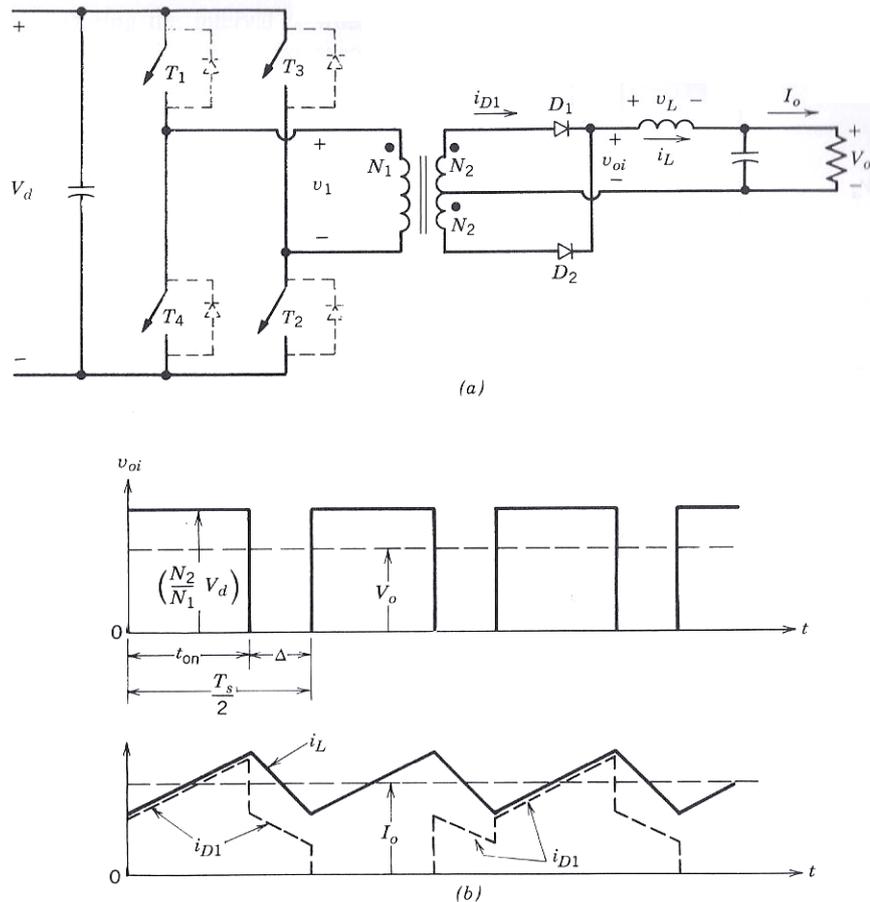

**Fig. 4: (a) Full-bridge converter. (b) voltage and current waveforms:  $i_L$  the current of the inductor,  $v_{oi}$  is the voltage from the left side of the inductor to the middle tap of the secondary winding.**

Figure 4 shows a full bridge converter where  $(T_1, T_2)$  and  $(T_3, T_4)$  are pairs of switches, switched together alternatively for a time  $t_{on}$  in a switching cycle  $T_s$  (what is the switching frequency?). After each pair is turned off, there is a time interval  $\Delta$  when all switches are "off". When either pair is "on",  $v_{oi} = (N_2/N_1)V_d$ , and therefore

$$v_L = \frac{N_2}{N_1}V_d - V_o, \quad 0 < t < t_{on}.$$

Similarly, when all switches are "off",  $v_{oi} = 0$  (assuming ideal diodes), and therefore

$$v_L = -V_o, \quad t_{on} < t < t_{on} + \Delta.$$

In steady state, no energy is accumulated in the inductor, hence the time integral of the inductor voltage over one switching cycle is zero. Since  $t_{on} + \Delta = \frac{1}{2}T_s$ , we obtain:

$$\frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D,$$

where  $D = t_{on}/T_s$  is the duty cycle (in this case,  $0 < D < 0.5$ ).

The figures are taken from: N. Mohan, T. M. Undeland and W. P. Robbins, Power electronics: converters, applications and design, 3rd ed., Hoboken, NY: John Wiley and Sons, Inc., 2003.